

High Dynamic Range Signal Conversion




Jorge Guilherme



□Outline


- Context
- Pipeline Architecture
- Design of a 15-bit 10 MS/s Pipeline ADC
- Design of a 9-bit 10MS/s Logarithmic Pipeline ADC
- Other Projects
 - ❖ DC-DC controller for Space Applications
 - ❖ Class D Audio Amplifier

ADSL modem structure

 


POTS and ADSL information channels

 - 255 subcarriers
- 14-bit QAM
- Up to 8.8 Mbit/s




System considerations

 Bit error rate probability as a function of SNR for 14 bit QAM




Simulation with white noise

 



- For ADSL a ber of 10^{-8} requires an SNR of 42 dB for 14QAM
- ADSL requires an 80-dB dynamic range ADC due to signal dynamics
(80 dB = 42dB QAM + 3dB margin + 15dB crest factor + 10dB AGC + 10dB crosstalk)


2 solutions



 


- Linear pipeline ADC with 13-bit resolution
- Logarithmic 9-bit ADC converter with a max SNR of 44.3 dB and 80 dB dynamic range

ADC Converter Types

  

 

   

MDAC

$$V_o = \begin{cases} \left(1 + \frac{C_s}{C_f}\right) V_i - \frac{C_s}{C_f} V_{ref} & \text{if } V_i > V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i & \text{if } -V_{ref}/4 \leq V_i \leq +V_{ref}/4 \\ \left(1 + \frac{C_s}{C_f}\right) V_i + \frac{C_s}{C_f} V_{ref} & \text{if } V_i < -V_{ref}/4 \end{cases}$$

Pipeline ADC Generic Model

Generic ADC Pipeline Model Generator/Evaluator

Simulation Conditions

- Change Random Seed Alw...
- Save Results
- Analyse INL/DNL
- Analyse FFT
- Sinusoidal Input
- Include Front-end Stage Distorti...
- Ideal Model
 - Ideal Capacitors
 - Ideal Opamps DC gain
 - Ideal Opamps Setting
 - Ideal Opamps Offset
 - Ideal Flash Comps Offset
 - Ideal Flash Comps Sensitivity
 - Ideal Thermal Noise
- Input Signal Attenuation
 - 0.1 dB Below Full Scale
 - 1 # Monte Carlo Runs

Ploting for Debug

- Enable Debug Plotting
- Stg1/SH
- Stg2
- Stg3
- Stg4
- Stg other
- Vref Charge Transfer

Distortion Parameters

HD2 [dB]	-100
HD3 [dB]	75
HD4 [dB]	-100
HD5 [dB]	-80
HD6 [dB]	-100
HD7 [dB]	-90

Pipeline Model Parameters Definition

Model Name: ad1603

Input Vector Break-Down: 1 2^3

Create New Model, Lock Model, Load Config., Run Model, Close All

Operating Temperature [K]: 30+273

Sampling Frequency [Hz]: 3e6

Fs/Fi: 4

Opamps Slew Rate [V/s]: 25000e7

Latch Duration [s]: 2e-9

Sampling Random Jitter [s]: 0

Noise Integration 0Hz-Fint [Hz]: Fs/2

Validate Input Vector Sizes, Use Sample & Hold, Auto Fill Input Vectors

ADC Architecture: 1 3.5 3.5 1.5 1.5 1.5 1.5 1.5 1.5 1.5 2

Unit Capacitors [fF]: 2000 1000 250 100 50 50 50 50 50 50 50

Opamp DC Gain [dB]: 110 110 75 75 70 60 60 60 60 60 60

Update Noise, Use Excess Noise Factor Parameter

Stgs ONoise Z [uV]: 5 393.3 541 737.3 737.3 737.3 737.3 737.3 737.3 708.4

Stgs ONoise XY [uV]: 5 393.3 541 737.3 737.3 737.3 737.3 737.3 737.3 737.3 708.4

XS Noise Factor Z: 1 1 1 3 3 3 3 3 3 3 3

XS Noise Factor XY: 1 1 1 3 3 3 3 3 3 3 3

Opamp Offset ImV/I: 0 0 0 0 0 0 0 0 0 0 0

Comps Offset I/V: f/16 Vref/16 Vref/16 Vref/16 Vref/16 Vref/16

Comps Noise [V]: 0.005 0.005 0.005 0.005 0.005 0.005 0.005 0.005

Stages Settling Precision [bit]: 16 16 14 12 12 8 8 8 8 8 8

Capacitor Mismatch Info

Cap Density vertical (Ca): 0.69e-15

Perimeter cap density (Cp): 0.15e-15


Capacitors area (Caparea): $((\sqrt{16 \cdot C_p^2 + 4 \cdot C_a \cdot C_{unit}} - 4 \cdot C_p) / (2 \cdot C_a))^2$

Estimated Cap Density (CapParea): Ca+Cp


Capacitor Sigma(deltaC/C): 0.805 / (sqrt(2 * Caparea) * 100)


Model Path: E:\Linux\CAD\Projects\CCDAFE01\ESA_CCDAFE01\Docs\Architecture_Analysis\Matlab_model

NOT_USED
Used_to_test_functions
adc3v1

 

 Architecture of the 15-bit 10MS/s self-calibrated pipeline ADC



 

$$V_{ndac} = \sqrt{\frac{16 \cdot K \cdot T \cdot Id \cdot Fn}{3 \cdot V_{od}}} \cdot R$$

$$V_{namp} = \sqrt{\frac{2}{3} \frac{K \cdot T}{C_c} \cdot \frac{1 + \frac{V_{dsat1}}{V_{dsat7}}}{f}}$$

Kelvin 1998

The resistors and the DAC inject large noise!

The DAC noise current is proportional to gm

$$V_r = \sqrt{4 \cdot K \cdot T \cdot Fn \cdot R}$$

$$Fn = \frac{\pi}{2} \cdot Fo = 70\text{MHz}$$

$$SNR = 10 \cdot \log \left(\frac{\frac{1}{2} \cdot \left(\frac{Vref}{2} \right)^2}{\frac{Vref^2}{12 \cdot 2^{2N}} + \frac{2 \cdot K \cdot T}{C} + 4 \cdot Vnamp^2 + 2 \cdot Vr^2 + 2 \cdot Vndac^2 + \frac{2 \cdot Vr^2 + 2 \cdot Vnamp^2}{32}} \right) \approx 79dB$$

Noise distribution by block

Trade off between power,
noise and resolution
obtained by program


Quantization	$\cong 26\%$
KT/C	$\cong 17\%$
Resistors	$\cong 20\%$
DAC	$\cong 16\%$
Amplifiers	$\cong 21\%$



$C = 10 \text{ pF}$
 $Cc = 10 \text{ pF}$
 $Idac = 1 \text{ mA}$
 $Rstring = 1000 \text{ ohm}$


Noise Bandwidth of a 2 pole system = 0.7854 F_o helps
reducing the noise from the DAC and resistors

 - Current steering DAC requirements: random errors
 - Current source sizing: $\text{std dev}(\Delta I/I) = 0.027\%$ for 13 bit linearity
 - $V_{od} = 0.76V \implies$ total current source DAC transistor area = 0.817 mm^2 , DAC area = 1.7 mm^2
 - Hierarchical symmetrical switching scheme used to compensate systematic errors



$$(WL)_{\min} = \frac{1}{2} \frac{A_{\beta}^2 + 4 \frac{A_{vt}^2}{V_{ovd}^2}}{\sigma^2 \left(\frac{\Delta I}{I} \right)}$$

DAC Output

 

DAC Layout



Main schematic of the amplifiers used in the S/H and residue amplifiers


□ The amplifiers were designed based on the noise allowed to it dependent on C_c

□ A telescopic cascode compensation topology was chosen to minimize power

□ From C_c and GBW we obtained the gm and current of the input differential pair



$$GBW = \frac{gm}{2\pi C_c}$$
 
$$H(s) = \frac{\frac{gm_1}{C2.CT^2} \cdot (gm_3.gm_9 - C2.Cc.s^2)}{s^3 + \frac{gm_3.(CL + Cc) - \beta.gm_1.Cc}{CT^2} \cdot s^2 + \frac{gm_3.gm_9.Cc}{C2.CT^2} \cdot s + \frac{\beta.gm_1.gm_3.gm_9}{C2.CT^2}}$$



$$V_{namp} = \sqrt{\frac{2}{3}} \frac{K \cdot T}{C_c} \cdot \frac{1 + \frac{V_{dsat1}}{V_{dsat7}}}{f}$$


$$CT = \sqrt{C1.CL + C1.Cc + CL.Cc}$$

  

Yield of a 6 bit flash for INL=0.5LSB


$$\sigma^2(V_{os}) = \frac{A_{vt}^2}{(WL)_i} + \frac{(V_{GS} - V_T)^2}{4} \cdot \frac{A_\beta^2}{(WL)_i} \approx \frac{A_{vt}^2}{(WL)_i}$$

ROM

 

b3	Decimal	Binary	Thermometer	Gray	Two's Complement
0	000	000	0000000	000	000
1	001	001	0000001	001	111
2	010	010	0000011	011	110
3	011	011	0000111	010	101
4	100	100	0001111	110	100
5	101	101	0011111	111	011
6	110	110	0111111	101	010
7	111	111	1111111	100	001


Figure 29.1 Comparison of digital input codes.

 

Area = 1.7 * 0.72 mm²

Comparator




 

Summary


Resolution	15 bit
Conversion rate	10 Ms/s
Power consumption	320 mW
Power supply	2.7-3.3V
Input range	1.1V
SNDR	77.2 dB
THD	84.8 dB
ENB	12.5 bit
DNL, $f_{IN} = 9.5$ kHz	1.5 LSB at 15-bit
INL, $f_{IN} = 9.5$ kHz	3.3 LSB at 15-bit
Chip area	3.23 mm * 4.75 mm
Core area	2.8 mm * 4.3 mm
Process technology	0.35 μ m CMOS single poly 5-metal

Full Converter Experimental Results

 


Full Converter Experimental Results

Measured INL

 


Measured DNL

 



Vdd=3.3V
Fs=1MHz
Fin=9.5kHz
Vin=1.1V

16 million samples


Auxiliary Blocks

 

  
$$V_{OUT} = V_{be_1} - \left(1 + \frac{R_2}{R_3}\right)V_{OS} + \frac{R_2}{R_3}V_T \ln\left(n\left(1 - \frac{V_{OS}}{I_{R2}R_2}\right)\right)$$



Bias current generation

 


V_{cm} Voltage

 


Reference Voltage

Classical Linear Pipeline Converter



 


□ The signal operations in the linear domain are replaced by their equivalent in the logarithmic domain


Linear Domain

 

Logarithmic Domain

   


Logarithmic pipeline ADC architecture

 


- ❑ Replacing the signal operations in the linear pipeline we obtain a logarithmic pipeline ADC.
- ❑ A k offset at the input extends the range down to zero due to the logarithmic characteristic.

Converter characteristic

 

Residue of first stage

 


- Converter characteristics for positive input signals.
- The squarer gives a parabolic characteristic to the residue


$$DR_{dB} = 20 \cdot \log_{10} \frac{1}{K \cdot \left(\left(\frac{1}{K} + 1 \right)^{\frac{1}{2^N - 1}} - 1 \right)}$$

$$SNR_{dB} = 10 \cdot \log_{10} \frac{3 \cdot 2^{2N}}{\ln \left(1 + \frac{1}{k} \right)}$$

□ Solution for bipolar characteristic

 


 - After first stage residue signal is always positive due to squarer.
- Following stages only process positive input signals.
- The sign bit is extracted by the intersection of the input stage characteristics.
- Second stage is split in two to allow the sign bit decision





Logarithmic pipeline ADC

1.5-bit pipeline stage block diagram

 

 Architecture of the 9-bit 10MS/s logarithmic pipeline ADC




 

Summary

Resolution	9 bit
Conversion rate	10 Ms/s
Power consumption	478 mW
Power supply	2.2-2.7V
Input range	1V
SNR	45.7 dB
Dynamic range	79.28 dB
Chip area	3.1 mm*2.6 mm
Process technology	0.25 μ m CMOS single poly 5-metal

 
Evaluation of the logarithmic pipeline ADC



Measured output of the pipeline converter by injecting a triangular waveform of 250 Hz at the input, for a clock frequency of 1.3 MHz

Other Projects

DC-DC Controller for Space Application

 


Radiation resistant isolated DC-DC converter using a forward topology


Controller Features

- **Current mode control, cycle by cycle current limit**
- **Up to 2nF drive capability (to drive external power MOS)**
- **Soft-Start**
- **External shutdown/enable pin**
- **Adjustable oscillator frequency (up to 2MHz) using a single resistor**
- **PFM control mode for light loads to improve efficiency**
- **Radiation hardening**
- **Technology AMS 035 um CMOS**


Controller:

 

 Area = 2.79 mm²
Technology: 0.35um CMOS C35B4C3 4M/2P/HR/5V IO **Integrated Prototype:**



Class-D Audio Amplifier

 


Results:

- THD below -92dB with 8ohm load at 680mW (~0.0025%)
- Over 26dB THD reduction when compared with open loop results
- $3.6\mu\text{V}_{\text{rms}}$ closed-loop base-band noise


Design Example – BTL Class-D

 THD simulation results for Class-D with and without filter feedback – Comparison between BTL and SE Amp.





Test-Chip Architecture

A Multi-mode Stereo Class-D Amplifier

 

Test-Chip Layout

  Fully differential BLT Class-D Amplifier – Single Channel (UMC 018 um)



Note: MPW area constrains TC to single channel (1 reticule, 1.52x1.52 mm²)

Summary

- A 15-bit 10MS/s pipeline ADC was presented
 - Linearity determined by matching accuracy of a current steering DAC.
 - A calibration scheme adjust the reference voltage of the backend pipeline, instead of calibrating the gain of the front-end stage.
- A 9-bit 10MS/s true logarithmic pipeline ADC derived from their linear counterparts.
 - Symmetrical characteristic with dynamic range independent of SNR
 - SNR of 44.3 dB for a dynamic range of 80 dB.
- Other Projects
 - DC-DC controller for Space Applications
 - Class D Audio Amplifier